

Elmore Delay

**Nachiket Kapre**  
nachiket@uwaterloo.ca




# Outline

- ▶ Simple RC network
- ▶ Elmore Delay Model
- ▶ Buffered Interconnect

# Delay Modeling

- ▶ Approximate delay models useful during FPGA/ASIC CAD optimization
- ▶ Chicken-egg problem: How to synthesize circuits for delay before placement/routing?
- ▶ Can we predict (to the first order) how fast a given design will run?
  - ▶ Can optimize and choose faster circuits during design space exploration
  - ▶ Heuristics can use predictions to throw out bad alternatives, focus on better options
- ▶ Wire delays are dominant, must model them properly to drive optimizations
- ▶ In software, compilers often use **profile-guided optimization** to generate better machine code. Since (1) FPGA CAD tools take very long, and (2) CAD heuristics produce noisy results, this has traditionally not been a sensible strategy.

# Analysis of simple RC Networks

 

- ▶ Simple series composition of voltage source + resistor + capacitor
- ▶ Apply Ohm's law  $V = I \cdot R$ , capacitor equation  $I = C \cdot \frac{dV}{dt}$ , and Kirchoff's voltage law  $\sum_i V_i = 0$

$$V_{src} - V_{res} - V_{cap} = 0$$

$$V_{src} - I \cdot R - V_{cap} = 0$$


$$V_{src} - C \cdot \frac{dV}{dt} \cdot R - V_{cap} = 0$$

$$V_{cap} = V_{src} - R \cdot C \cdot \frac{dV}{dt}$$

$$V_{cap} = V_{src} \cdot (1 - e^{\frac{-t}{R \cdot C}})$$


- ▶ Time constant  $= \tau = R \cdot C$
 
## Impact of $\tau$ on charging profiles of capacitor




- ▶ Different RC time constants deliver different charging profiles
  - ▶ Assume unit of  $\tau = \Omega \cdot F$ , unit of time is  $s$
  - ▶ Typically, we design circuits to run at 100s of MHz, so time is in  $ns \rightarrow$  RC should be in  $k\Omega \cdot pF$  range.
- ▶ The RC time constant represents time at which  $V_{cap}$  gets 63% of its final value.

## Why are we doing this?

 


- ▶ When drawing timing diagrams we assume square waves, or gently sloping slanting edges
- ▶ Real life is *analog* with smoother curves → gate voltages have thresholds to detect logic 0s and 1s,
- ▶ Can we still deliver proper voltage behavior at gate inputs in the prescribed clock period in presence of analog effects?

## Why are we doing this?

 

- ▶ When drawing timing diagrams we assume square waves, or gently sloping slanting edges
- ▶ Real life is *analog* with smoother curves → gate voltages have thresholds to detect logic 0s and 1s,
- ▶ Can we still deliver proper voltage behavior at gate inputs in the prescribed clock period in presence of analog effects?

## Why are we doing this?

 


- ▶ When drawing timing diagrams we assume square waves, or gently sloping slanting edges
- ▶ Real life is *analog* with smoother curves → gate voltages have thresholds to detect logic 0s and 1s,
- ▶ Can we still deliver proper voltage behavior at gate inputs in the prescribed clock period in presence of analog effects?



## Timing Analysis with $\tau$


- ▶ Static Timing Analysis (STA) identifies longest paths in your circuit and adds up delays of components along the path
  - ▶ Exception of false paths which are not activated.
- ▶ However, this only considers logic delays
- ▶ Modern chips, 80–90% of delay is in wiring
- ▶ Wires can be modeled as RC networks → but can we estimate delay without solving differential equations?

## Static Timing Analysis (revisited)

 


- ▶ Using STA, we calculated critical path as the **blue** edge
- ▶ With delay analysis, our job is to annotate each edge with a number corresponding to wire delay
- ▶ Possible to consider delay through wire as linearly proportional to length. **Wrong**

## Static Timing Analysis (revisited)

 

- ▶ Using STA, we calculated critical path as the **blue** edge
- ▶ With delay analysis, our job is to annotate each edge with a number corresponding to wire delay
- ▶ Possible to consider delay through wire as linearly proportional to length. **Wrong**
 
## Analysis of marginally more complex RC Networks



- Apply KVL to find unknown voltage  $V_2$

$$V_{src} - V_{R_1} - V_{R_2} - V_2 = 0 \quad (1)$$

$$V_{src} - (I_1 + I_2) \cdot R_1 - I_2 \cdot R_2 - V_2 = 0 \quad (2)$$

$$V_{src} - I_1 \cdot R_1 - I_2 \cdot (R_1 + R_2) - V_2 = 0 \quad (3)$$

$$V_{src} - C_1 \cdot \frac{dV_1}{dt} \cdot R_1 - C_2 \cdot \frac{dV_2}{dt} \cdot (R_1 + R_2) - V_2 = 0 \quad (4)$$

- No closed form solution exists!

## Elmore Delay Analysis

- ▶ Interconnect on chips can be modeled as a collection of RC trees → need to setup complex differential equations!
- ▶ **Solution:** Elmore delay allows us to consider both these effects by assuming that change in voltage at all nodes is identical. *i.e.*  $\frac{dV_1}{dt} = \frac{dV_2}{dt}$

$$V_{src} - C_1 \cdot \frac{dV_1}{dt} \cdot R_1 - C_2 \cdot \frac{dV_2}{dt} \cdot (R_1 + R_2) - V_2 = 0$$



$$V_{src} - C_1 \cdot \frac{dV}{dt} \cdot R_1 - C_2 \cdot \frac{dV}{dt} \cdot (R_1 + R_2) - V_2 \approx 0$$

$$V_{src} - \frac{dV}{dt} \cdot (C_1 \cdot R_1 + C_2 \cdot (R_1 + R_2)) - V_2 \approx 0$$

$$V_2 \approx V_{src} - \frac{dV}{dt} \cdot (C_1 \cdot R_1 + C_2 \cdot (R_1 + R_2))$$



$$V_2 \approx V_{src} \cdot \left(1 - e^{\frac{-t}{C_1 \cdot R_1 + C_2 \cdot (R_1 + R_2)}}\right)$$

## Analyzing a net

  


- ▶ A **net** is a wire with one source and multiple destinations.
- ▶ Replace each wire segment with an RC model
- ▶ Each net becomes a **tree** of RC components that **approximately** model the timing behavior of the physical implementation
- ▶ Important: Trees do not have cycles

## Analyzing a net

  

- ▶ In practice, wire segments are shared during signal routing
- ▶ Must decompose the net into a series of segments
- ▶ Replace each segment with an RC model

# The Elmore Delay Equation

 

- ▶ The RC structure is the building block used in construction of RC trees
  - ▶ Model interconnect as a hierarchy of wire segments
  - ▶ Common use case: output of gate connected to inputs of several other gates
  - ▶ If you find loops, or feedback edges in the resulting network, you are doing something wrong
- ▶ To compute delay through  $R_i$ , you must consider **all** the capacitance seen at the output node  $i$  of the building block
  - ▶ For a tree, all sub-tree capacitances must be added. Simply  $\sum_k C_k$  for all  $k$  connected to  $i$ .

- ▶  $T_i = T_{R_i} = R_i \cdot \sum_k C_{ik}$
- ▶  $T_{path} = \sum_i (R_i \cdot \sum_k C_{ik})$




## Analyzing a net (substitute values)

- Analyze each segment along  $V_x \rightarrow V_3$  path

- $t_{V_x \rightarrow V_3} = t_{R_1} + t_{R_2} + t_{R_3}$
- $t_{R_1} = R_1 \cdot (C_1 + C_2 + C_3 + C_4 + C_5)$
- $t_{R_2} = R_2 \cdot (C_2 + C_3 + C_5)$
- $t_{R_3} = R_3 \cdot C_3$

- Analyze others paths

 - $t_{V_x \rightarrow V_2} = R_1 \cdot (C_1 + C_2 + C_3 + C_4 + C_5) + R_2 \cdot (C_2 + C_3 + C_5) + R_5 \cdot C_5$
- $t_{V_x \rightarrow V_1} = R_1 \cdot (C_1 + C_2 + C_3 + C_4 + C_5) + R_4 \cdot C_4$




## Analyzing a net (substitute values)

- Analyze each segment along  $V_x \rightarrow V_3$  path

- $t_{V_x \rightarrow V_3} = t_{R_1} + t_{R_2} + t_{R_3}$
- $t_{R_1} = R_1 \cdot (C_1 + C_2 + C_3 + C_4 + C_5)$
- $t_{R_2} = R_2 \cdot (C_2 + C_3 + C_5)$
- $t_{R_3} = R_3 \cdot C_3$

- Analyze others paths

 - $t_{V_x \rightarrow V_2} = R_1 \cdot (C_1 + C_2 + C_3 + C_4 + C_5) + R_2 \cdot (C_2 + C_3 + C_5) + R_5 \cdot C_5$
- $t_{V_x \rightarrow V_1} = R_1 \cdot (C_1 + C_2 + C_3 + C_4 + C_5) + R_4 \cdot C_4$




## Analyzing a net (substitute values)

- Analyze each segment along  $V_x \rightarrow V_3$  path

- $t_{V_x \rightarrow V_3} = t_{R_1} + t_{R_2} + t_{R_3}$
- $t_{R_1} = R_1 \cdot (C_1 + C_2 + C_3 + C_4 + C_5)$
- $t_{R_2} = R_2 \cdot (C_2 + C_3 + C_5)$
- $t_{R_3} = R_3 \cdot C_3$

- Analyze others paths

 - $t_{V_x \rightarrow V_2} = R_1 \cdot (C_1 + C_2 + C_3 + C_4 + C_5) + R_2 \cdot (C_2 + C_3 + C_5) + R_5 \cdot C_5$
- $t_{V_x \rightarrow V_1} = R_1 \cdot (C_1 + C_2 + C_3 + C_4 + C_5) + R_4 \cdot C_4$




## Analyzing a net (substitute values)

- Analyze each segment along  $V_x \rightarrow V_3$  path

- $t_{V_x \rightarrow V_3} = t_{R_1} + t_{R_2} + t_{R_3}$
- $t_{R_1} = R_1 \cdot (C_1 + C_2 + C_3 + C_4 + C_5)$
- $t_{R_2} = R_2 \cdot (C_2 + C_3 + C_5)$
- $t_{R_3} = R_3 \cdot C_3$

- Analyze others paths

 - $t_{V_x \rightarrow V_2} = R_1 \cdot (C_1 + C_2 + C_3 + C_4 + C_5) + R_2 \cdot (C_2 + C_3 + C_5) + R_5 \cdot C_5$
- $t_{V_x \rightarrow V_1} = R_1 \cdot (C_1 + C_2 + C_3 + C_4 + C_5) + R_4 \cdot C_4$




## Analyzing a net (substitute values)

- Analyze each segment along  $V_x \rightarrow V_3$  path


- $t_{V_x \rightarrow V_3} = t_{R_1} + t_{R_2} + t_{R_3}$
- $t_{R_1} = R_1 \cdot (C_1 + C_2 + C_3 + C_4 + C_5)$
- $t_{R_2} = R_2 \cdot (C_2 + C_3 + C_5)$
- $t_{R_3} = R_3 \cdot C_3$

- Analyze others paths

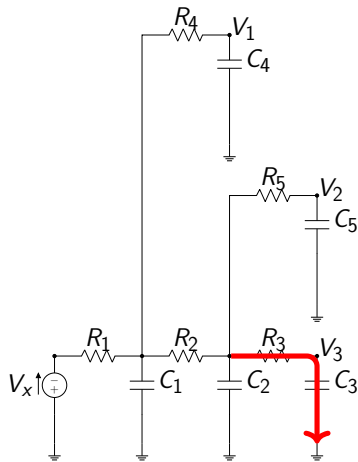- $t_{V_x \rightarrow V_2} = R_1 \cdot (C_1 + C_2 + C_3 + C_4 + C_5) + R_2 \cdot (C_2 + C_3 + C_5) + R_5 \cdot C_5$
- $t_{V_x \rightarrow V_1} = R_1 \cdot (C_1 + C_2 + C_3 + C_4 + C_5) + R_4 \cdot C_4$




## Static Timing Analysis (re-revisited)

 

- ▶ When assuming equal delay per gate, and zero wire delay, we may think the blue critical path goes through the most number of gates → 2 NOT gates, 1 AND gate + 1 OR gate
- ▶ After Elmore delay analysis of paths, maybe  $x \rightarrow \text{and}_1$  connection makes that the critical path!

## Static Timing Analysis (re-revisited)

 


- ▶ When assuming equal delay per gate, and zero wire delay, we may think the blue critical path goes through the most number of gates  $\rightarrow$  2 NOT gates, 1 AND gate + 1 OR gate
- ▶ After Elmore delay analysis of paths, maybe  $x \rightarrow and_1$  connection makes that the critical path!

# Buffered Interconnect

- ▶ Wire delays are dominant in modern chips – FPGAs and ASICs
- ▶ A chip typically is a 3D stack of multiple metal layers + logic layers at the bottom
- ▶ Shorter wires typically use lower levels for routing, Longer wires in upper levels
- ▶ Wire cross sections look pretty unusual in modern chips



## RC model of long wires

 

- ▶ We know long wires are slower than shorter wires, but by how much?
- ▶ Long wires can be broken down into series of RC blocks
- ▶ Each RC block models the delay behavior of a *unit length* wire segment
- ▶  $R_l$  and  $C_l$  are resistance and capacitance per unit length

## RC model of long wires

- ▶ Applying Elmore delay model to this network with  $N$  segments, we can write:
- ▶ For first segment,  $T_0 = R_l \cdot \sum_{i=0}^{N-1} C_l$  generalizes to  $\rightarrow T_j = R_l \cdot \sum_{i=j}^{N-1} C_l$
- ▶  $T_{V_{src} \rightarrow V_{dest}} = R_l \sum_{i=0}^{N-1} C_l + R_l \sum_{i=1}^{N-1} C_l + R_l \sum_{i=2}^{N-1} C_l + \dots + R_l \sum_{i=N-1}^{N-1} C_l$


$$\begin{aligned} T_{V_{src} \rightarrow V_{dest}} &= \sum_{j=0}^{N-1} T_j \\ &= \sum_{j=0}^{N-1} R_l \sum_{i=j}^{N-1} C_l \\ &= R_l \cdot C_l \sum_{j=0}^{N-1} \sum_{i=j}^{N-1} 1 \\ &= R_l \cdot C_l \cdot \sum_{j=0}^{N-1} (N - j) \\ &= R_l \cdot C_l \cdot N * (N + 1) / 2 \\ &= O(N^2) \end{aligned}$$

## Wire delay growth

- ▶ Wire delay grows as  $O(N^2)$  where  $N$  is length of the wire
- ▶ This is bad, as you need to (1) pipeline longer wires, causing redesigns of your FSMs + delays + area (2) there is a poor upper limit of performance for fixed cost
- ▶ Buffering is one strategy to combat wire delay growth
- ▶ With proper selection of buffer count and strength, we can make wire delay grow linearly  $O(N)$ .
- ▶ Linear growth is the ideal scaling factor  $\rightarrow$  still only asymptotic
 
## Optimal Buffer Placement

- ▶ Buffers (pair of inverters) can help boost signal strength along the wire
- ▶ Effect of inserting a buffer = isolation of the capacitive load along the wire
- ▶ Elmore delay must be analyzed for the buffered wire segment + capacitive load of buffer



## Elmore Delay of Buffered Interconnect

$$T_{V_{src} \rightarrow V_{buf}} = \sum_{j=0}^{j=\frac{N}{k}-1} T_j$$
$$= R_l \cdot C_l \cdot \frac{N}{k} * (\frac{N}{k} + 1)/2$$

$$T_{V_{src} \rightarrow V_{dest}} = k \cdot (T_{V_{src} \rightarrow V_{buf}} + T_{buf})$$
$$= k \cdot (R_l \cdot C_l \cdot \frac{N}{k} * (\frac{N}{k} + 1)/2) + (k - 1) \cdot T_{buf}$$

- ▶ Assume the wire of length  $N$  segments is buffered  $k$  times *i.e.* at intervals of  $\frac{N}{k}$  segments
- ▶ Delay within the buffered segment follows  $O(N^2)$  scaling trend but  $N$  is now  $\frac{N}{k} \rightarrow k$  is a constant, so the asymptote is still quadratic
- ▶ Each buffer has its own input capacitance  $C_b$  which contributes to charging time of  $T_{buf}$  (No need to analyze  $C_b$  separately)
- ▶ How many segments  $k$  will deliver minimum total delay  $T_{V_{src} \rightarrow V_{dest}}$ ?

## Understanding delay extremes of buffered interconnect

- Expression for delay of buffered wire:

$$T_{V_{src} \rightarrow V_{dest}} = k \cdot (R_I \cdot C_I \cdot \frac{N}{k} * (\frac{N}{k} + 1)/2) + (k - 1) \cdot T_{buf}$$

- **Case 1:**  $k = N$ , provide a buffer every RC block

$$\begin{aligned} T_{V_{src} \rightarrow V_{dest}} &= N \cdot (R_I \cdot C_I \cdot \frac{N}{N} * (\frac{N}{N} + 1)/2) + (k - 1) \cdot T_{buf} \\ &= N \cdot (R_I \cdot C_I) + (N - 1) \cdot T_{buf} \end{aligned}$$

- **Case 2:**  $k = 1$ , no buffer at all, i.e. unbuffered

$$\begin{aligned} T_{V_{src} \rightarrow V_{dest}} &= 1 \cdot (R_I \cdot C_I \cdot \frac{N}{1} * (\frac{N}{1} + 1)/2) + (1 - 1) \cdot T_{buf} \\ &= (R_I \cdot C_I \cdot N \cdot (N + 1)/2) \end{aligned}$$

## Choosing the best $k$

- Expression for delay of buffered wire:

$$T_{V_{src} \rightarrow V_{dest}} = (R_I \cdot C_I \cdot (\frac{N^2}{k} + 1)/2) + (k - 1) \cdot T_{buf}$$

- **Case 3:**  $T$  is minimized when  $\frac{dT}{dk} = 0$

$$\frac{dT}{dk} = -(R_I \cdot C_I \cdot (\frac{N^2}{k^2})/2) + T_{buf}$$

$$0 = -(R_I \cdot C_I \cdot (\frac{N^2}{k^2})/2) + T_{buf}$$

$$R_I \cdot C_I \cdot (\frac{N^2}{k^2})/2 = T_{buf}$$

$$R_I \cdot C_I \cdot (\frac{N^2}{T_{buf}})/2 = k^2$$

$$k = N \cdot \sqrt{R_I \cdot C_I / 2 \cdot T_{buf}}$$

## Delay at best $k$

- ▶ Expression for delay of buffered wire:  $T_{V_{src} \rightarrow V_{dest}} \approx (R_l \cdot C_l \cdot (\frac{N^2}{k})/2) + (k) \cdot T_{buf}$

$$T_{V_{src} \rightarrow V_{dest}} \approx (R_l \cdot C_l \cdot (\frac{N^2}{N \cdot \sqrt{R_l \cdot C_l / 2 \cdot T_{buf}} + 1})/2) + (N \cdot \sqrt{R_l \cdot C_l / 2 \cdot T_{buf}}) \cdot T_{buf}$$

- ▶ Substituting  $k$

$$\approx (R_l \cdot C_l \cdot (\frac{N}{\sqrt{R_l \cdot C_l / 2 \cdot T_{buf}}})/2) +$$

$$(N \cdot \sqrt{R_l \cdot C_l \cdot T_{buf} / 2})$$

$$\approx N \cdot (\sqrt{R_l \cdot C_l \cdot T_{buf} / 2}) +$$

$$(N \cdot \sqrt{R_l \cdot C_l \cdot T_{buf} / 2})$$

- ▶ Delay is minimized when delay through RC tree = delay through buffers!



## Class Wrapup

- ▶ Elmore Delay Model replaces the need for solving complex differential equations to compute time
- ▶ Represent nets are **trees** of distributed RC elements
- ▶ STA (Static Timing Analysis) must include Elmore delay calculations for accurate assesment of circuit performance
- ▶ Buffering of long wires uses Elmore delay-driven analysis