

# FPGA Logic

**Nachiket Kapre**

nachiket@uwaterloo.ca




## Lecture Outline

- ▶ **PLAs and LUTs** – Beginning of programmable logic fabrics
- ▶ **LUT Clusters** – Need for packing multiple LUTs together

# Properties of Circuits


- ▶ Expressed as collection of boolean gates connected by wires
  - ▶ Arithmetic operations typically not expressed at gate-level
- ▶ Flexibility in choices of gate + pattern of wire connections
- ▶ Reconvergent fanout
- ▶ Pipelining (periodic insertion of registers)

## Early Configurable Logic

 


- ▶ PLAs (programmable logic arrays) provide some configurability
- ▶ Each crosspoint is programmable
  - ▶ Visualize a truth table overlayed on top of the AND crosspoints
- ▶ The number of pterms is often  $\ll 2^{\text{inputs}}$ .
  - ▶ A  $k$ -LUT, in contrast can support  $2^k$  pterms with no extra cost
- ▶ PLAs are cheaper/simpler starting points

## Implement poly on a PLA

 




- ▶ Logic equation to map:  
$$a \cdot x \cdot x + b \cdot x + c = a \cdot x + b \cdot x + c$$
- ▶ Problem has 4 Inputs, 3 Product Terms, One Output
- ▶ Map two expression to the AND plane
  - ▶  $and0 = a \cdot x \cdot x = a \cdot x$
  - ▶  $and1 = b \cdot x$
  - ▶  $and2 = c$
- ▶ Map the final result to the OR plane
  - ▶  $y0 = and0 + and1 + and2$

## Logic Elements

 

- ▶ Boolean table mapped to Configuration cells (SRAMs, or fuses).
- ▶  $k$ -input table has  $2^k$  cells.
- ▶ Actel FPGAs have cheaper one-time use fuses.
- ▶ Tabula failed at using deeper configuration memories (circuit changes per cycle)
- ▶ Samsung/Stanford DRAM-based FPGAs (must worry about refresh)

## Logic Elements (Pass gates)

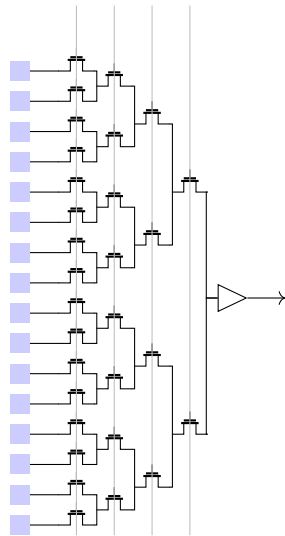  

select lines are alternately  
inverted

## Area/Delay Estimates


- ▶ 
$$A_{LUT} = A_{Config} * 2^k + A_{Mux} * (2^k - 1) + A_{FF}$$
$$\approx 2^k * (A_{Config} + A_{Mux}) + A_{FF}$$
  - ▶  $2^k$  cells are configured as RAMs
  - ▶ Need  $2^k - 1$  muxes as well
  - ▶ An SRAM cell typically needs 6–8 transistors
  - ▶ A pass-gate implementation of 2:1 Mux takes 2 transistors
  - ▶ A DFF takes 16 transistors
  - ▶ Depending on load, larger transistors needed
- ▶  $T_{LUT} = k \cdot T_{Mux}$ 
  - ▶  $k$  levels of multiplexer hierarchy



## How to choose $k$ ?

- ▶ If  $k$  is too small, a large gate must be split across multiple LUTs.
  - ▶ Increases area used by circuit
  - ▶ Adds delay due to composition of multiple LUTs
  - ▶ Interconnect is expensive, absorb wires where you can
- ▶ If  $k$  is too large, need to allocate silicon area for  $2^k$  SRAM cells.
  - ▶ Logic synthesis may generate gates that are at most 7 or 8-input
  - ▶ Most gates may be 2-input (distribution varies with application, logic synthesis optimizations)
  - ▶ Underutilization of silicon area due to over-provisioning of LUT capacity
 
## Mapping poly to LUTs for different goals



### ► $k=3 \rightarrow$ two LUTs

- $A_{k=3} = 2 \cdot A_{3LUT} = 2 \cdot (A_{Config} * 2^3 + A_{Mux} * (2^3 - 1) + A_{FF}) = 16 * A_{Config} + 14 * A_{Mux} + 2 * A_{FF}$

- $T_{k=3} = 2 \cdot T_{3LUT} = 2 \cdot 3 \cdot T_{Mux} = 6 \cdot T_{Mux}$

### ► $k=4 \rightarrow$ one LUT

- $A_{k=4} = A_{4LUT} = A_{Config} * 2^4 + A_{Mux} * (2^4 - 1) + A_{FF} = 16 * A_{Config} + 15 * A_{Mux} + A_{FF}$

- $T_{k=4} = T_{4LUT} = 4 \cdot T_{Mux}$


- $A_{k=3} - A_{k=4} = A_{FF} - A_{Mux}$

- $T_{k=3} - T_{k=4} = 2 \cdot T_{Mux}$


# Clustering FPGA LUTs into Logic Blocks

- ▶ Exposing  $k$  LUTs creates  $k+1$  connections between logic and routing.
  - ▶ Can we reduce this without sacrificing connectivity?
  - ▶ Real-world circuits exhibit locality anyway. Can we exploit this?
- ▶ Increasing  $k$  costs us FPGA area ( $2^k$  SRAM cells).
- ▶ Clusters are small collections of  $N$  LUTs with separate local interconnect
  - ▶ Pay  $N \cdot 2^{k_{small}}$  area cost instead of  $2^{k_{large}}$ .
  - ▶ Assume some inputs are common to the  $N$   $k_{small}$  LUTs. Thus we do not need  $N \cdot k_{small}$  IOs from cluster.
  - ▶ Intra-cluster wires as faster, and can be richer
  - ▶ CAD is faster as it can be split into global and local phases

# Clustering FPGA LUTs into Logic Blocks

 

# Clustering FPGA LUTs into Logic Blocks

 

## Area Estimates

- ▶  $A_{Cluster} = N * A_{kLUT} + A_{Green} + A_{Red}$
- ▶  $A_{Green} = N * k * (N - k + 1) * A_{sw}$ 
  - ▶ Output needs to connect to any one input of k-LUT
  - ▶ LUT inputs are all equivalent, sufficient to provide connection to single LUT pin
- ▶  $A_{Red} = k * N * M * A_{sw}$ 
  - ▶ Internal routing block (Red) is a crossbar.
  - ▶ In the worse case,  $M = k * N$
  - ▶ Typical value  $M = \frac{k}{2} * (N + 1)$
- ▶  $A_{sw} = A_{config} + A_{Mux}$

## Putting it all together $A_{Cluster}$

$$\begin{aligned}A_{Cluster} &= N * A_{kLUT} + A_{Green} + A_{Red} \\&= N \cdot (2^k \cdot A_{Config} + 2^k \cdot A_{mux} + A_{FF}) + N \cdot k \cdot (N - k + 1) \cdot (A_{Config} + A_{Mux}) \\&\quad + k \cdot N \cdot M \cdot (A_{Config} + A_{mux}) \\&= N \cdot (2^k \cdot A_{Config} + 2^k \cdot A_{mux} + A_{FF}) + N \cdot k \cdot (N - k + 1) \cdot (A_{Config} + A_{Mux}) \\&\quad + k \cdot N \cdot \frac{k}{2} \cdot (N + 1) \cdot (A_{Config} + A_{mux}) \\&= N \cdot (2^k + k \cdot (N - k + 1) + \frac{(N + 1) \cdot k^2}{2}) \cdot A_{Config} \\&\quad + N \cdot (2^k + k \cdot (N - k + 1) + \frac{(N + 1) \cdot k^2}{2}) \cdot A_{mux} + N \cdot A_{FF}\end{aligned}$$

- ▶ Area of the cluster scales as a function of  $k$ ,  $N$  and  $M$
- ▶ Substituting terms from previous slides, we get a result that grows as  $O(N^2 \cdot k^2)$

## External Interconnect (Peek)

- ▶ Area of Grey region will be covered in detail in the Interconnect lecture.
- ▶  $A_{Gray} = M * W * F_{cin} * A_{sw} + N * W * F_{cout} * A_{sw}$
- ▶ External routing block (cbox) is partially connected with  $F_{cin}$  and  $F_{cout}$  parameters
- ▶  $W$  is the global channel width of the FPGA *i.e.* number of wires in the global interconnect channel beside the cluster



## How to choose cluster size $N$ ?

- ▶ If  $N$  is too small, we do not offload sufficient wiring costs in the global interconnect.
  - ▶ If connectivity between cluster to routing tracks is poor, we will waste LUTs that are unreachable
- ▶ If  $N$  is too large, the intra-cluster routing area can become prohibitively expensive
- ▶ How do we choose  $N$  to balance these effects?

## Class Wrapup

- ▶ Underling FPGA resources can be modeled using a simple analytical approach
- ▶ Heuristic/Experimental technique to determine best balance between  $N$  and  $k$  parameters of the resource model
- ▶ Example of engineering tradeoff → more compute, or more interconnect?