

# State Machine Examples


**Nachiket Kapre**  
nachiket@uwaterloo.ca



# Outline


- ▶ Complex control flow in state machines
- ▶ FSMD Pattern  $\rightarrow$  Finite State Machine + Datapath

## Example 4: Counter with skip option

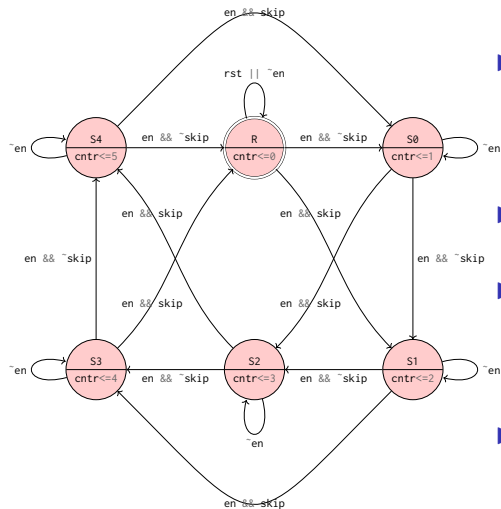


- ▶ **Problem:** design a counter that counts from 0 to 5, and restarts from 0. Counter updates only on enable, and skips by 2 if skip input is enabled!
- ▶ Number of states = 6, 1-bit enable input, 1-bit skip input, Output = 3-bit count
- ▶ Three kinds of state transitions
  - ▶ Normal advancement if en **and** ~skip
  - ▶ Jump if en && skip
  - ▶ Self loop if ~en
- ▶ Each state has a simple action to assign a constant value to cntr output

## Example 4: Counter with skip option


 


- ▶ **Problem:** design a counter that counts from 0 to 5, and restarts from 0. Counter updates only on enable, and skips by 2 if skip input is enabled!
- ▶ Number of states = 6, 1-bit enable input, 1-bit skip input, Output = 3-bit count
- ▶ Three kinds of state transitions
  - ▶ Normal advancement if `en` **and** `~skip`
  - ▶ Jump if `en && skip`
  - ▶ Self loop if `~en`
- ▶ Each state has a simple action to assign a constant value to `cntr` output

## Example 4: FSM Diagram

 


## Example 4: Counter with skip option

 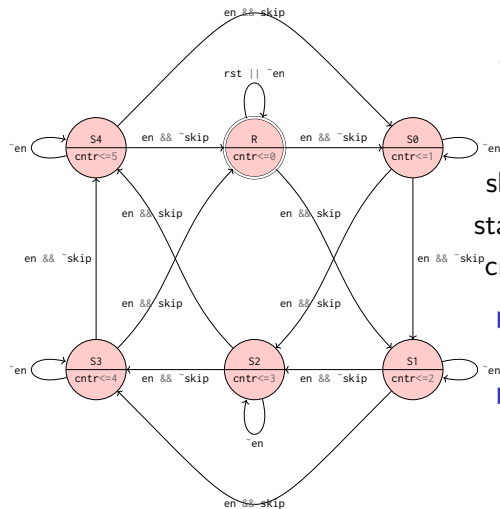


- ▶ Now have inputs en and skip in the timing diagram
- ▶ Each State has three outgoing edges →
  - ▶ Either, only one condition must be true
  - ▶ Or use nested if to infer priority

## Example 4: Counter with skip option

 

```
module cnt5enskip(  
    input wire clk,  
    input wire rst,  
    input wire en,  
    input wire skip,  
    output reg [2:0] cnt  
);
```

## Example 4: Counter with skip option

 


Nested if  
but mutually exclusive

```
R : begin //
    if(en && ~skip) begin
        state <= S0;
    end
    else if(en && skip) begin
        state <= S1;
    end //
end
```

Missing Else  
Stay in same state




## Example 4: Counter with skip option

 


```
always @(posedge clk) begin
  if(rst) begin
    cntr <= 0;
  end else begin
    case(state)
      R : cntr <= 0;
      S0 : cntr <= 1;
      S1 : cntr <= 2;
      S2 : cntr <= 3;
      S3 : cntr <= 4;
      S4 : cntr <= 5;
    endcase
  end
end
```
 
## Example 5: Counter with up/down option




- ▶ **Problem:** design a counter that counts from 0 to 5, and restarts from 0. Counter updates only on enable, and supports reversing count.
- ▶ Number of states = 6, 1-bit enable input, 1-bit up/down input, Output = 3-bit count
- ▶ Three kinds of state transitions
  - ▶ Normal advancement if `en && up`
  - ▶ Reverse flow if `en && ~up`
  - ▶ Self loop if `~en`
- ▶ Each state has a simple action to assign a constant value to cnt output
 
## Example 5: Counter with up/down option




- ▶ **Problem:** design a counter that counts from 0 to 5, and restarts from 0. Counter updates only on enable, and supports reversing count.
- ▶ Number of states = 6, 1-bit enable input, 1-bit up/down input, Output = 3-bit count
- ▶ Three kinds of state transitions
  - ▶ Normal advancement if `en && up`
  - ▶ Reverse flow if `en && ~up`
  - ▶ Self loop if `~en`
- ▶ Each state has a simple action to assign a constant value to `cntr` output
 
## Example 5: Counter with up/down option





- ▶ **Problem:** design a counter that counts from 0 to 5, and restarts from 0. Counter updates only on enable, and supports reversing count.
- ▶ Number of states = 6, 1-bit enable input, 1-bit up/down input, Output = 3-bit count
- ▶ Three kinds of state transitions
  - ▶ Normal advancement if `en && up`
  - ▶ Reverse flow if `en && ~up`
  - ▶ Self loop if `~en`
- ▶ Each state has a simple action to assign a constant value to cnt output

## Example 5: FSM Diagram

 

  
## Example 5: Counter with up/down option




- ▶ Now have inputs en and up in the timing diagram
- ▶ Each State has three outgoing edges →
  - ▶ Again, mutual exclusivity or priority must be enforced
 
## Example 5: Counter with up/down option



```
module cnt5updown(  
    input wire clk,  
    input wire rst,  
    input wire en,  
    input wire up,  
    output reg [2:0] cnt  
);
```
 
## Example 5: Counter with up/down option




Nested if  
but mutually exclusive

```
R : begin //  
  if(en && up) begin  
    state <= S0;  
  end else if(en && ~up) begin  
    state <= S4;  
  end //  
end
```

Missing Else  
Stay in same state


 
## Example 5: Counter with up/down option




Nested if  
but mutually exclusive

```
R : begin //  
  if(en && up) begin  
    state <= S0;  
  end else if(en && ~up) begin  
    state <= S4;  
  end //  
end
```

Missing Else  
Stay in same state
 
## Example 5: Counter with up/down option



```
always @(posedge clk) begin
  if(rst) begin
    cntr <= 0;
  end else begin
    case(state)
      R : cntr <= 0;
      S0 : cntr <= 1;
      S1 : cntr <= 2;
      S2 : cntr <= 3;
      S3 : cntr <= 4;
      S4 : cntr <= 5;
    endcase
  end
end
```


## RTL Coding Impact of skip/up input

- ▶ Each state now has multiple outgoing edges
  - ▶ The condition to activate each edge should be mutually exclusive
  - ▶ If that is not possible, there should be a priority order
    - ▶ This may be denoted with a separate priority label on each edge
    - ▶ Makes the FSM diagram complicated, so generally avoided
- ▶ Diagrams can get messy → anticipate congestion, space things apart



## Two interacting state machines

- ▶ **Problem:** Design a *cascaded* counter which contains a pair of upstream and downstream counters.
  - ▶ The upstream counter counts from 0 to 5 in a free-running manner. When it overflows, it restarts, and generates an enable signal for the downstream counter for one cycle. This tells the downstream counter to increment by 1.
  - ▶ The downstream counter also counts from 0 to 5 in a conditional manner based on an enable signal generated by the upstream counter.
- ▶ Number of FSMs=2
  - ▶ FSM1: Number of states = 6, no input, Output = 3-bit count + 1-bit overflow
  - ▶ FSM2: Number of states = 6, 1-bit enable input, Output = 3-bit count
- ▶ Interacting state machines with unidirectional flow of data


## Rough sketch of design

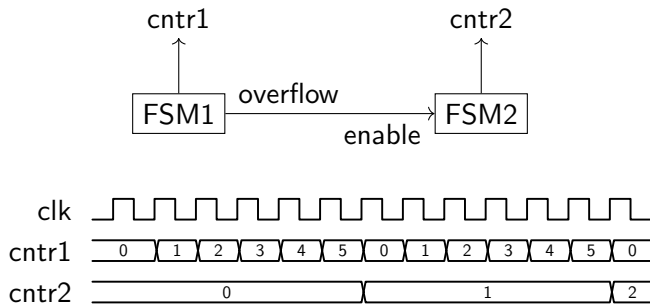

## Two interacting state machines

  

# Timing Diagram

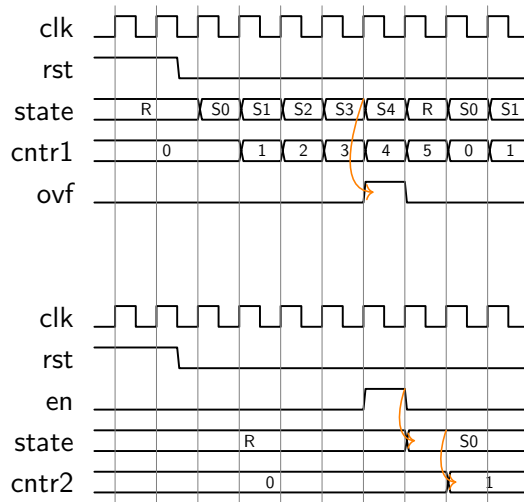

## Explanation


- ▶ Generate overflow a cycle sooner to allow cntr values to align
- ▶ Direction of dataflow is from FSM1 to FSM2
  - ▶ Output ovf from FSM1 is input en for FSM2
- ▶ FSM1 is just a free-running counter from before, with special signal to indicate overflow
  - ▶ Note that overflow indication will be generated a cycle after the state, hence assigned as state action in S4.
- ▶ FSM2 will see one-cycle enable signals, so state machine will advance at a much slower rate



# FSMD Design Pattern


- ▶ FSMs can drive Datapath logic
- ▶ Datapaths contain arithmetic units, logic blocks, muxes, stitched together in dataflow fashion
- ▶ FSMs can control and co-ordinate data movement in datapaths
- ▶ FSMs can decide when inputs enter, and when outputs leave a Datapath

# FSMD: Finite State Machine + Datapath

 

- ▶ Typically **FSMs** drive a Time-multiplexed **Datapath**
- ▶ FSM generates control signals to orchestrate use of datapath blocks in each cycle
- ▶ e.g. In a processor
  - ▶ The instruction decoder + program counter can be an **FSM**
  - ▶ ALU with multiplexers and bypassing logic is the **Datapath**
- ▶ FSM generates a multiplexer control table

# Datapath

 

```


wire [7:0] add_mux_c;
wire [15:0] mult_mux_c;
wire [23:0] add_c;
wire [23:0] mult_c;
reg [23:0] temp1;

// output register and mux
always @(posedge clk) begin
    if(rst) begin
        temp1 <= {24{1'b0}};
    end else begin
        if((op == 1'b 0)) begin
            temp1 <= add_c;
        end else begin
            temp1 <= mult_c;
        end
    end
end


// arithmetic ops
assign add_c = add_mux_c + temp1;
assign mult_c = mult_mux_c * x;
assign y = temp1;

// input muxes
assign add_mux_c = add_in == 1'b 0 ? b : c;
assign mult_mux_c = mult_in == 1'b 0 ?
    {8'b 00000000,a} : temp1[15:0];
    
```


## Cycle-by-cycle operation

 


## Cycle-by-cycle operation

 


## Cycle-by-cycle operation

 

## Cycle-by-cycle operation

 


## Cycle-by-cycle operation

 



# Poly State Machine

 

- ▶ Datapath will compute  $a \cdot x^2 + b \cdot x + c$
- ▶ State machine will control order of operation and generation of output
- ▶ Approximately a simple CPU structure (state = program counter)
- ▶ Internal state  $t$  separate from the state variable

# Poly FSMD in Verilog (only FSM)

```
always @(posedge clk) begin
  if(rst) begin
    state <= STEP0;
  end else begin
    case(state)
      STEP0 : begin
        state <= STEP1;
      end
      STEP1 : begin
        state <= STEP2;
      end
      STEP2 : begin
        state <= STEP3;
      end
      STEP3 : begin
        state <= STEP0;
      end
    endcase
    y_valid <= y_valid_c;
  end
end
```

```
always @(*) begin
  mult_in <= 1'b 0;
  add_in <= 1'b 0;
  y_valid_c <= 1'b 0;
  case(state)
    STEP0 : begin
      op <= 1'b 1; // *
      mult_in <= 1'b 0; // A
    end
    STEP1 : begin
      op <= 1'b 0; // +
      add_in <= 1'b 0; // B
    end
    STEP2 : begin
      op <= 1'b 1; // *
      mult_in <= 1'b 1; // TEMP
    end
    STEP3 : begin
      op <= 1'b 0; // +
      add_in <= 1'b 1; // C
      y_valid_c <= 1'b 1;
    end
  endcase
end
```

# Parenthesis Matching Problem

- ▶ . . . ( . . . ( ) ( ) ( ( ) ) . . . )
- ▶ Check if the expression is balanced
  - ▶ Simply counting ( and ) won't do
  - ▶ Can we do this with a state machine?

# Wrapup

- ▶ Finite State Machines can have complex control flow with multiple branches from each state → must consider priority or mutual exclusivity
- ▶ FSMs can interact with each other → must pay attention to cycle/timing of interacting signals
- ▶ FSMs key component of the FSMD design pattern!
- ▶ FSMs are everywhere: communication chips, crypto, games, ...