

# State Machines

**Nachiket Kapre**


nachiket@uwaterloo.ca



# Outline

- ▶ Need for state machines
- ▶ Kinds of state machines in hardware
- ▶ Drawing waveforms + RTL coding styles

## Why is state necessary?

 


- ▶ CS theory tells us about Turing Machines!
  - ▶ Infinite tape (memory) + FSM (finite-state machine)
- ▶ (1) State (infinite tape) is a pre-requisite to compute any function that is computable! → Yes, state is necessary for computation
  - ▶ Not just that, it must be **infinite**!
- ▶ (2) FSMs here have **finite** state and manage/control the computation

# State Machines in Software

- ▶ **Trivial case:** In software, for loops implicitly use state-machines.
  - ▶ Loop counter is the state
  - ▶ In each state, execute body of the loop
  - ▶ Update loop counter (state) and repeat
  - ▶ JUMP or BRANCH instruction is your state transition
- ▶ **Event-driven design:** Repetitive, iterative tasks need control management
  - ▶ Systematic way to reason about ordering of events
  - ▶ Define rules governing which states are allowed
  - ▶ Potentially avoid logical bugs → assert states you can never enter
  - ▶ e.g.: Device drivers, IO protocols are examples of state machines
 
# Implicit State Machines in C

```
for(int i=0; i<N; i++) {  
    y[i]=a[i]*x[i]*x[i]+b[i]*x[i]+c[i];  
}
```



- ▶ For loops are simplest state machines in C
  - ▶ Three states: Initial, Update, Terminate
  - ▶ **Initial:** `int i=0`
  - ▶ **Update:** compute `y[i]`, `i++`
  - ▶ **Terminate:** `i==N-1`
- ▶ Conveniently pack specification of all states, transition operations in one line of code
  - ▶ `for(int i=0; i<N; i++)`
- ▶ Can visually represent them as a graph (nodes = states, edges = state transitions)

## The story so far...



- ▶ Combinational logic is stateless (memoryless), composed of logic gates, arithmetic operations, and wires
- ▶ Registers add state. But, we have only covered **feed-forward** design → data flows in one direction only!
- ▶ Fundamental new idea in state machine design is that of **feed-back** → data can flow backwards in a particular manner!

## The story so far...



- ▶ Combinational logic is stateless (memoryless), composed of logic gates, arithmetic operations, and wires
- ▶ Registers add state. But, we have only covered **feed-forward** design → data flows in one direction only!
- ▶ Fundamental new idea in state machine design is that of **feed-back** → data can flow backwards in a particular manner!

# Feedforward vs. Feedback

**One Direction = Feedforward**




**Jimi Hendrix's guitar = Feedback**






# High-Level View of State Machines

 


- ▶ Presence of feedback fundamental to the idea of state machines
- ▶ State machines are a powerful abstraction for reasoning about computation in presence of feedback

## High-Level View of State Machines

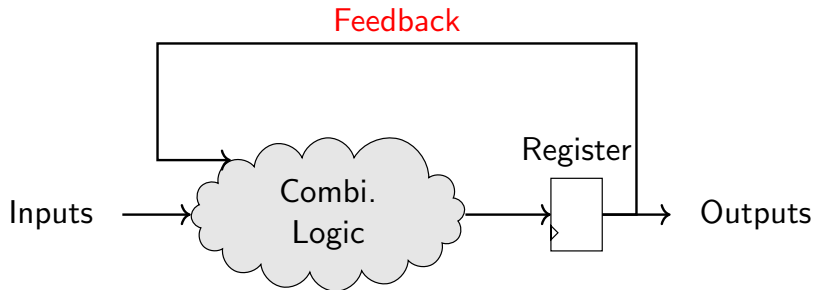


- ▶ Presence of feedback fundamental to the idea of state machines
- ▶ State machines are a powerful abstraction for reasoning about computation in presence of feedback

# High-Level View of State Machines

 


- ▶ Optionally the output computation may pass through another stage of combination logic + register
- ▶ Possible (not recommended) option to use inputs directly to compute outputs

# High-Level View of State Machines

 

- ▶ Optionally the output computation may pass through another stage of combination logic + register
- ▶ Possible (not recommended) option to use inputs directly to compute outputs

# High-Level View of State Machines

 


- ▶ Optionally the output computation may pass through another stage of combination logic + register
- ▶ Possible (not recommended) option to use inputs directly to compute outputs

# Learning Goals

- ▶ How to draw a state machine?
  - ▶ Reason about correctness/performance here!
- ▶ How to draw a timing diagram for a state machine?
  - ▶ Expect a certain behavior of your computation
- ▶ How to implement the state machine in RTL
  - ▶ Write RTL last! Once you have a visual representation + waveform analysis

# Notation

 


- ▶ Each state is a node in the graph – pack both state name + state action (if present) in the same bubble.
- ▶ Each transition is an edge in the graph – pack both condition (if present) and state action (if present) in the same edge.
- ▶ Show reset state with double circle (or other shape with two borders)

# Recipe for State-Machine Engineering in Hardware

- ▶ 1. Choose number of states you need for your problem
- ▶ 2. Define state transition conditions clearly between states
- ▶ 3. Identify what actions happen in each state (or transition)
- ▶ 4. Check if your machine is correct →
  - ▶ Does it get stuck in a state and never comes out (unless that is by design)
  - ▶ Is a state never reachable? Dead code. Wasting states+area
  - ▶ Check for causality → time travel is strictly forbidden
- ▶ 5. Optimize for performance →
  - ▶ Use **one-hot** encoding of state bits. Needs a bit more registers, but reduces decoder cost
  - ▶ If outputs go to different module/RTL developer, they may come back saying register this signal → An extra cycle of delay requires redesign of states
  - ▶ Actions on transitions could have a slight performance penalty





## Example 1: Free-running count to 5

 


- ▶ **Problem:** design a counter that counts from 0 to 5, and restarts from 0, running forever
- ▶ Number of states = 6, No inputs, Output = 3-bit count
- ▶ State transitions have no conditions, no actions  
→ state machine will transition between states on each clock
- ▶ Each state has a simple action to assign a constant value to cntr output

## Example 1: Free-running count to 5

  


- ▶ State labels shown directly in the data bundles for state row
- ▶ Output of state machine trails the state by one cycle, as outputs are registered!
  - ▶ If output is combinational (not recommended), it will coincide with the state

## Example 1: Free-running count to 5


 


 Counter output  
trails state  
by one cycle





- ▶ State labels shown directly in the data bundles for state row
- ▶ Output of state machine trails the state by one cycle, as outputs are registered!
  - ▶ If output is combinational (not recommended), it will coincide with the state

## Example 1: Free-running count to 5

  


- ▶ State labels shown directly in the data bundles for state row
- ▶ Output of state machine trails the state by one cycle, as outputs are registered!
  - ▶ If output is combinational (not recommended), it will coincide with the state

## Example 1: Free-running count to 5

  


- ▶ State labels shown directly in the data bundles for state row
- ▶ Output of state machine trails the state by one cycle, as outputs are registered!
  - ▶ If output is combinational (not recommended), it will coincide with the state

## Example 1: Free-running count to 5

 


- ▶ State labels shown directly in the data bundles for state row
- ▶ Output of state machine trails the state by one cycle, as outputs are registered!
  - ▶ If output is combinational (not recommended), it will coincide with the state

## Example 1: Free-running count to 5

 

```
module cnt5 (  
    input wire clk,  
    input wire rst,  
    output reg [2:0] cnt  
);
```


## Example 1: Free-running count to 5

 

```
enum {R,S0,S1,S2,S3,S4} state; //
```




## Example 1: Free-running count to 5

 

Enumerated  
SystemVerilog type


```
enum {R,S0,S1,S2,S3,S4} state; //
```

## Example 1: Free-running count to 5

 

```
always@(posedge clk) begin: run_stmc
  if (rst) begin
    state <= R; //
  end else begin
    case (state)
      R      : state <= S0;
      S0     : state <= S1;
      S1     : state <= S2;
      S2     : state <= S3;
      S3     : state <= S4;
      S4     : state <= R;
      default : state <= R; //
    endcase
  end
end
```


## Example 1: Free-running count to 5

 

```
always@(posedge clk) begin: run_stmc
  if (rst) begin
    state <= R; //
  end else begin
    case (state)
      R      : state <= S0;
      S0     : state <= S1;
      S1     : state <= S2;
      S2     : state <= S3;
      S3     : state <= S4;
      S4     : state <= R;
      default: state <= R; //
    endcase
  end
end
```

Ensure state machine starts in sensible state


## Example 1: Free-running count to 5

 

```
always@(posedge clk) begin: run_stmc
  if (rst) begin
    state <= R; //
  end else begin
    case (state)
      R      : state <= S0;
      S0     : state <= S1;
      S1     : state <= S2;
      S2     : state <= S3;
      S3     : state <= S4;
      S4     : state <= R;
      default : state <= R; //
    endcase
  end
end
```


Default not necessary  
for enum types

## Example 1: Free-running count to 5

 

```
always@(posedge clk) begin: compute
  if (rst) begin
    cntr <= 0;
  end else begin
    case (state)
      R      : cntr <= 0; //
      S0     : cntr <= 1;
      S1     : cntr <= 2;
      S2     : cntr <= 3;
      S3     : cntr <= 4;
      S4     : cntr <= 5;
      default : cntr <= 0;
    endcase
  end
end
```

## Example 1: Free-running count to 5

 


```
always@(posedge clk)
if (rst) b
  cntr <= 0;
end else begin
  case (state)
    R      : cntr <= 0; //
    S0     : cntr <= 1;
    S1     : cntr <= 2;
    S2     : cntr <= 3;
    S3     : cntr <= 4;
    S4     : cntr <= 5;
    default : cntr <= 0;
  endcase
end
end
```

Registered action  
per state

# RTL Coding Guidelines for State Machines

- ▶ An RTL state machine needs a `clk` and a `rst`
- ▶ It may have multiple (or no) inputs, but will generally have at least one output
- ▶ Reset self loop need not be shown (assume its there)
- ▶ State decoder block is a separate always block → `run_stmc:` block in our code example
- ▶ Output decoder block is its own block → `compute:` block in our code example
- ▶ We used `case` statement since the state machine cannot be in two states at the same time
- ▶ No `others` clause required as the state enumeration is exhaustive → do not forget a state


 
## Example 2: Externally enabled count to 5



- ▶ **Problem:** design a counter that counts from 0 to 5, and restarts from 0, running forever. Count updates only on enable!
- ▶ Number of states = 6, 1-bit enable input, Output = 3-bit count
- ▶ Two kinds of state transitions
  - ▶ Normal advancement if en
  - ▶ Self loop if ~en
- ▶ Each state still has a simple action to assign a constant value to cntr output




  
## Example 2: Externally enabled count to 5





- ▶ Input en advances state machine
- ▶ State stops changing a cycle after en goes low
- ▶ Output trails the state by one cycle.
- ▶ Output stabilizes two cycles after en goes low
  
## Example 2: Externally enabled count to 5





- ▶ Input en advances state machine
- ▶ State stops changing a cycle after en goes low
- ▶ Output trails the state by one cycle.
- ▶ Output stabilizes two cycles after en goes low
  
## Example 2: Externally enabled count to 5




- ▶ Input en advances state machine
- ▶ State stops changing a cycle after en goes low
- ▶ Output trails the state by one cycle.
- ▶ Output stabilizes two cycles after en goes low
  
## Example 2: Externally enabled count to 5




- ▶ Input en advances state machine
- ▶ State stops changing a cycle after en goes low
- ▶ Output trails the state by one cycle.
- ▶ Output stabilizes two cycles after en goes low
 
## Example 2: Externally enabled count to 5




```
module cnt5en (  
    input wire clk,  
    input wire rst,  
    input wire en,  
    output reg [2:0] cnt  
);
```
 
## Example 2: Externally enabled count to 5



```
always@(posedge clk) begin : run_stmc
  if (rst) begin
    state <= R;
  end else begin
    case (state)
      R      : if (en) state <= S0;
      S0     : if (en) state <= S1;
      S1     : if (en) state <= S2;
      S2     : if (en) state <= S3;
      S3     : if (en) state <= S4;
      S4     : if (en) state <= R;
      default : state <= R;
    endcase
  end
end
```
 
## Example 2: Externally enabled count to 5




```
always@(posedge clk) begin : compute
  if (rst) begin
    cntr <= 0;
  end else begin
    case (state)
      R      : cntr <= 0;
      S0     : cntr <= 1;
      S1     : cntr <= 2;
      S2     : cntr <= 3;
      S3     : cntr <= 4;
      S4     : cntr <= 5;
      default : cntr <= 0;
    endcase
  end
end
```

## RTL Coding Impact of en input

- ▶ Input is only read in the `run_stmc:` block
  - ▶ This block advances the state machine
  - ▶ Nested `if` statements inside a `case` statement
  - ▶ Processing of `~en` is not explicit
  - ▶ Missing `else` will cause state to hold onto its current value.
- ▶ Output decoder block block → `compute:` is unchanged!!
- ▶ Separation of input processing and output generation
- ▶ Note the one cycle delay required to reflect input change on state
- ▶ And the second cycle delay required to reflect state change on output change



 
### Example 3: Externally enabled count to 5 with fast out





- ▶ **Problem:** design a counter that counts from 0 to 5, and restarts from 0, running forever. Count updates only on enable! Result is available sooner!
- ▶ Number of states = 6, 1-bit enable input, Output = 3-bit count
- ▶ Two kinds of state transitions
  - ▶ Normal advancement if en
  - ▶ Self loop if ~en
- ▶ Each state still has a simple action to assign a constant value to cntr output
 
### Example 3: Externally enabled count to 5 with fast out





- ▶ **Problem:** design a counter that counts from 0 to 5, and restarts from 0, running forever. Count updates only on enable! Result is available sooner!
- ▶ Number of states = 6, 1-bit enable input, Output = 3-bit count
- ▶ Two kinds of state transitions
  - ▶ Normal advancement if en
  - ▶ Self loop if ~en
- ▶ Each state still has a simple action to assign a constant value to cntr output
  
### Example 3: Externally enabled count to 5 with fast out





- ▶ Now have faster update to cntr in the timing diagram
- ▶ This is possible by modifying output decoder to check both input and state
  - ▶ By predicting the next state value, output can be sped up by one cycle to change in-sync with the state
  
### Example 3: Externally enabled count to 5 with fast out



- ▶ Now have faster update to cntr in the timing diagram
- ▶ This is possible by modifying output decoder to check both input and state
  - ▶ By predicting the next state value, output can be sped up by one cycle to change in-sync with the state
  
### Example 3: Externally enabled count to 5 with fast out




- ▶ Now have faster update to cntr in the timing diagram
- ▶ This is possible by modifying output decoder to check both input and state
  - ▶ By predicting the next state value, output can be sped up by one cycle to change in-sync with the state

Output **nsync** with state


 
### Example 3: Externally enabled count to 5 with fast out



```
case(state)
```

```
...
```

```
R : if(en) state <= S0; //
```

```
...
```

```
endcase
```

```
case(state)
```

```
...
```

```
R : begin
```

```
  cntr <= 0;
```

```
  if(en) cntr <= 1;
```

```
end //
```

Unconditional  
state transition

Action while  
changing state!

## RTL Coding Impact of faster output

- ▶ Output can be made to align with state transition
  - ▶ Requires modification to the compute block to include **if** condition
  - ▶ Again, nested **if** statements inside a **case** statement
  - ▶ Output will acquire default value assigned at start of state → hence **else** not needed and still OK!
  - ▶ Ignoring the **else** on the output will infer unwanted state on the output registers.
- ▶ Thus, single cycle delay from input to state as well as input to output.
- ▶ **Effect:** More complex output decoder design, can often be slower in frequency



# Wrapup

- ▶ State Machines are a **compact** way to represent computation with some notion of memory or state (feedback)
- ▶ RTL offers a rich set of patterns to express state machines with clocked+combinational blocks
- ▶ Design challenge is to identify how many states you need, and to determine if actions happen inside a state, or along an edge