

Pipelining Examples and Back-Pressure

Nachiket Kapre
nachiket@uwaterloo.ca



UNIVERSITY OF
WATERLOO

Outline

- ▶ Throughput Handling
- ▶ Why do we need rate control
- ▶ Types of control
 - ▶ Global stall signal
 - ▶ Registered stage-by-stage stall


Pipelining with low-throughput components

- ▶ Not always possible to *fully pipeline* the datapath for high throughput
 - ▶ Some components naturally take multiple cycles to complete
→ shift-add multiplier
 - ▶ Sometimes you run out of resources
- ▶ For these components, computation is sequential →
Throughput T is inverse of Latency L .
 - ▶ Range of throughputs possible $\frac{1}{L} \leq T \leq 1$
 - ▶ Even lower throughputs possible if some internal state clearing logic is activated
- ▶ **Q** Can we check if our design is balanced? Are we over or under pipelining our hardware?
 - ▶ It is all about equalizing throughput!

Throughput Balancing through Replication


- ▶ Shift-add multiplier takes 8 cycles to perform an 8×8 multiplication \rightarrow each cycle is a shift-and-add operation
- ▶ Throughput= $\frac{1}{8}$, Latency=8
- ▶ You are required to boost throughput of the design but do not have manpower to rewrite RTL for a new multiplier architecture

Throughput Balancing through Replication

 


- ▶ Perform $a \times b = c$ on inputs arriving each cycle
- ▶ Replicate the shift-and-add multiplier $8\times$ to boost throughput.
- ▶ Add 1:8 demultiplexer at input to distribute inputs to the eight components
 - ▶ A demux is often just a wire with valid signals
- ▶ An 8:1 multiplexer at the output collects results from each block
- ▶ A 3-bit counter drives the select lines of mux and demux structures

Replication Waveforms

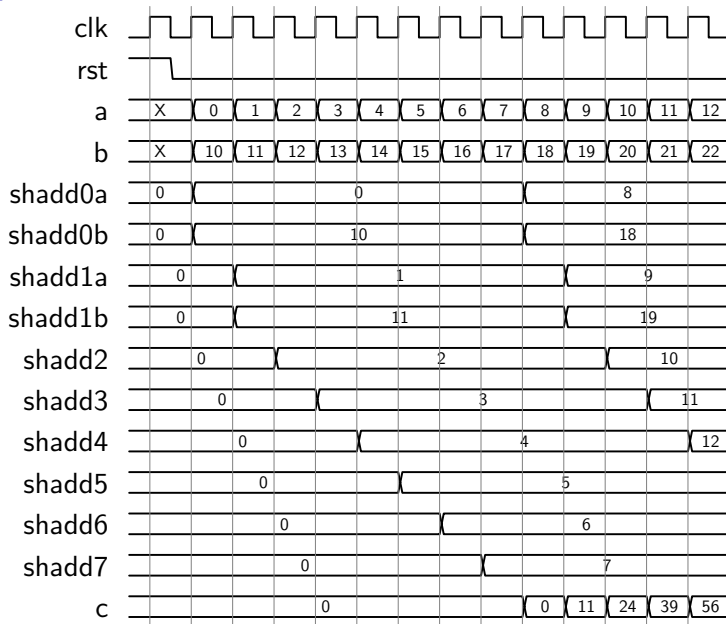

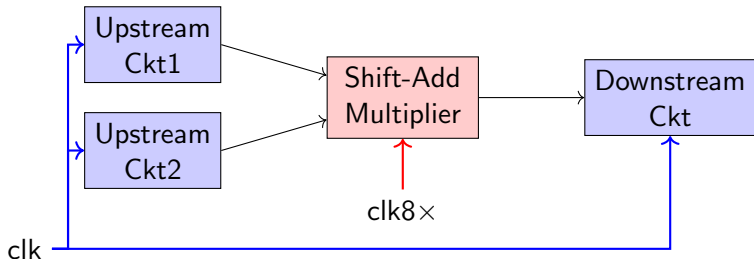Throughput Balancing through Clock Domains




- ▶ Supply two different clocks (phase aligned, integer multiples)
- ▶ Shift-Add runs at fast $8\times$ clock \rightarrow one cycle for the upstream/downstream circuits is 8 cycles for a shift add!
- ▶ In general, crossing clock domains is like crossing countries \rightarrow you need a passport, visas, Here, we need synchronizers or asynchronous FIFOs (out of scope of 627)

EIGHT CYCLES OF SHIFT-ADD (CLK8X)

ARE WORTH ONE CYCLE OF IO (CLK1X)

imgflip.com

Clock Domain Crossing Waveforms

 

Controlling data transfers

- ▶ Valid signaling is useful for one-way communication of information
- ▶ Most hardware designs use standard handshake protocols requiring bidirectional dataflow
 - ▶ Valid bit from sender to receiver
 - ▶ Ready bit from receiver to sender
- ▶ Standard bus interfaces such as AXI (Advanced Extensible Interface) part of AMBA (ARM Advanced Microcontroller Bus Architecture) support valid + ready handshake