

# FPGA Interconnect

**Nachiket Kapre**

nachiket@uwaterloo.ca




# Lecture Outline

- ▶ **Wiring and Switching** – Costs and tradeoffs
- ▶ **Putting it together** – sbx and cbox model

# Properties of Communication in Circuits


- ▶ Wiring in circuits connect gates and registers to each other
  - ▶ Persistent connection. Even if data doesn't change.
- ▶ Locality of connectivity.
  - ▶ Do not need all-to-all connectivity.
  - ▶ Input equivalence at LUT
  - ▶ Fewer long connections, More short connections.
- ▶ Wiring area and delay dominate overall circuit behavior
 
## Relative cost of Logic and Interconnect




- ▶ Efficient to decompose large-input functions into lots of small LUTs + wires
  - ▶ Large LUT area scales as  $2^k_{large}$
  - ▶ Alternative:  $N \times 2^k_{small} + A_{interconnect}$
- ▶ Even with added expense of wires ( $A_{interconnect}$ ), still better than  $2^k_{large}$
- ▶ Interconnect area for *programmable logic* has two components:
  - ▶ Wires
  - ▶ Programmable Switches

## Directional Crosspoint

 


- ▶ A crosspoint for directional wires is one transistor + one SRAM cell
- ▶ Can also be visualized as a 2:1 mux driven by the two wires and controlled by the SRAM cell
- ▶ Hence,  $A_{sw} = A_{Config} + A_{Mux}$

## Limits of crossbar

 


- ▶ Over-provisions connectivity
- ▶  $O(N)$  wires in the bisection
  - ▶  $N$  wires in horizontal and vertical cuts
  - ▶ 2D layout  $O(N^2)$  wiring area
- ▶  $O(N^2)$  switches
- ▶ What dominates? (1) wires or (2) switches
  - ▶  $\lambda$  is a unit of length defined by the manufacturing technology *i.e.* 32 nm, 18 nm, 7 nm.
  - ▶ Wire pitch (spacing between wires)  $\approx 10\lambda$ 
    - ▶ Wire area for  $N$  wires is  $(N \times 10\lambda)^2 = N^2 \times 100\lambda^2$
  - ▶ Switch area (2:1 mux+SRAM cell) is  $1000\lambda^2$ 
    - ▶ Switch area for  $N^2$  switches is  $N^2 \times 1000\lambda^2$
  - ▶ Switch area ( $N^2 \times 1000\lambda^2$ )  $\gg$  Wire area ( $N^2 \times 100\lambda^2$ )

# Interconnect of Modern FPGAs

 

- ▶ Island-style FPGAs used by Xilinx/Altera
  - ▶ Each island is a LUT cluster (from last lecture)
  - ▶ Also called CLB (Configurable Logic Block)
- ▶ **Switch-box (sbox)**: allows horizontal and vertical traffic to turn
- ▶ **Connection-box (cbox)**: allows wires to enter/exit CLB


# Interconnect of Modern FPGAs

 

- ▶ Parameters of interest
  - ▶  $W$  is channel width (number of wires in horizontal/vertical tracks)
  - ▶ Recall,  $M = \frac{k}{2} * (N + 1)$ , number of inputs to CLB
- ▶ **Connectionbox** parameters
  - ▶  $F_{cin}$  is the fraction of  $W$  tracks connected to  $M$  CLB inputs
    - ▶ Recall,  $M = \frac{k}{2} * (N + 1)$
  - ▶  $F_{cout}$  is the fraction of  $W$  tracks connected to  $N$  LUT outputs
- ▶ **Switchbox** parameters
  - ▶  $F_s$  is the number of switches connected to each wire at input of sbox



# Connection-box Architecture (cbox)

 


## ► Switch Area calculation

- Num. switches =  
 $M * W * F_{cin} + N * W * F_{cout}$
- Cbox Area =  
 $(W * M * F_{cin} + W * N * F_{cout}) * 1000\lambda^2$
- At 10%,  $W * (M + N) * 100\lambda^2$

- Wiring cost is a function of  $W * M$  dictated by  $10\lambda$  pitch

- $(W * 10\lambda) * ((M + N) * 10\lambda)$
- $W * (M + N) * 100\lambda^2$

# Switch-box Architecture (sbox)

 


## ► Switch Area

- Switch count =  $W \times F_s \times 2$
- Switch area =  $W * F_s * 2 * 1000\lambda^2 = W * 6000\lambda^2$


- Wiring cost is a function of  $O(W^2)$  dictated by  $10\lambda$  pitch
  - $(W * 10\lambda) * (W * 10\lambda)$
  - $W^2 * 100\lambda^2$
- wire dominated at  $W > 60$

# Diamond Crosspoint

 


- ▶ A diamond switchbox works for bidirectional wires
- ▶ Six possible links (fanout is also allowed)
- ▶ Need a new SRAM cell for each link
- ▶ Hence,  $A = 6 * A_{sw} = 6 * (A_{Config} + A_{Mux})$
 
# Understanding diamond crosspoints (Xilinx XC4000s)




- ▶ Each diamond crosspoint (switch) is actually 6 transistors + 6 SRAM cells (one per wire)
- ▶ If we have  $W$  channels, we need one diamond crosspoint per wire
- ▶ Naive crossbar will have  $W^2$  switches, but we only have  $W$  switches
- ▶ Same crosspoint can route two independent routes!
 
# Understanding diamond crosspoints (Xilinx XC4000s)




- ▶ Each diamond crosspoint (switch) is actually 6 transistors + 6 SRAM cells (one per wire)
- ▶ If we have  $W$  channels, we need one diamond crosspoint per wire
- ▶ Naive crossbar will have  $W^2$  switches, but we only have  $W$  switches
- ▶ Same crosspoint can route two independent routes!
 
## Understanding diamond crosspoints (Xilinx XC4000s)



- ▶ Each diamond crosspoint (switch) is actually 6 transistors + 6 SRAM cells (one per wire)
- ▶ If we have  $W$  channels, we need one diamond crosspoint per wire
- ▶ Naive crossbar will have  $W^2$  switches, but we only have  $W$  switches
- ▶ Same crosspoint can route two independent routes!
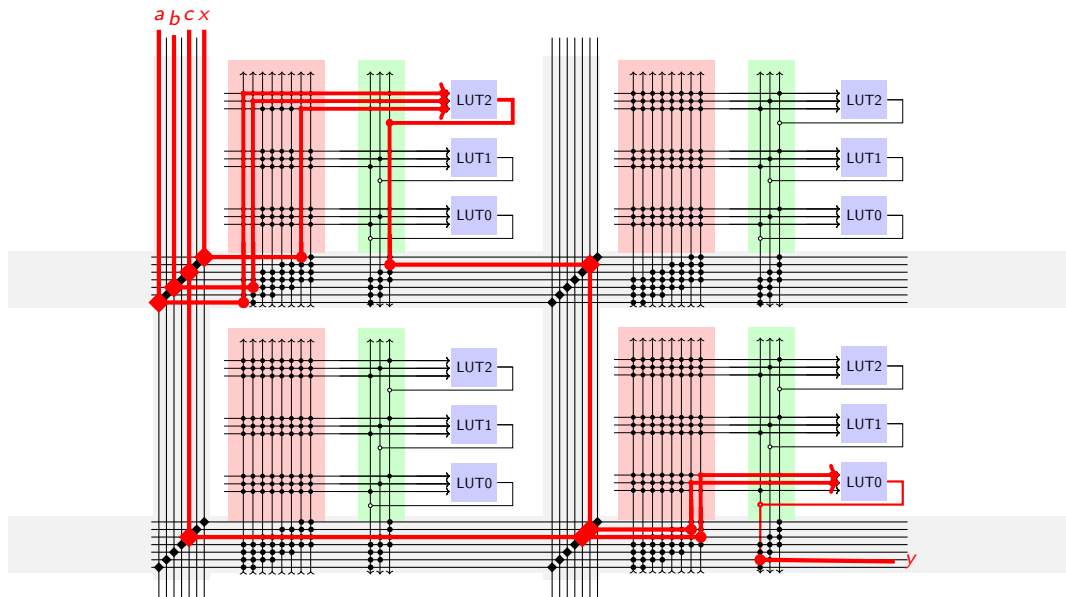
## Putting it together (LUTs + Cluster + Global)



## Relative Areas

- ▶ Logic Area (Assume  $A_{Config} + A_{Mux} = 1000\lambda^2$ ,  $A_{FF} = 0$ )
  - ▶  $N * A_{kLUT} = N * (2^k * A_{Config} + 2^k * A_{Mux})$
  - ▶  $(2^k * N) * 1000\lambda^2$
- ▶ Interconnect Area (Assume  $A_{Config} + A_{Mux} = 1000\lambda^2$ )
  - ▶ Intra-Cluster Area
    - ▶ Output Area =  $k * N * (N - k + 1) * A_{sw}$
    - ▶ Input Area =  $k * N * M * A_{sw}$
    - ▶  $k^2 * N * (N - k + 1 + M) * 1000\lambda^2 \approx N^2 * \frac{k^2}{2} * 1000\lambda^2$
  - ▶ Cbox Area (Assume  $F_{cin} = F_{cout} = 10\%$ )
    - ▶ Switch Area =  $M * W * F_{cin} * A_{sw} + N * W * F_{cout} * A_{sw}$
    - ▶ Wiring Area =  $(W * 10\lambda) * ((M + N) * 10\lambda)$
    - ▶  $\max(W * (M + N) * 100\lambda^2, W * (M + N) * 100\lambda^2) \approx W * \frac{k}{2} * N * 100\lambda^2$
  - ▶ Sbox Area (Assume  $F_s=3$ )
    - ▶ Switch Area =  $W * F_s * 2 * 1000\lambda^2$
    - ▶ Wiring Area =  $(W * 10\lambda) * (W * 10\lambda)$
    - ▶  $\max(W * 6000\lambda^2, W^2 * 100\lambda^2) \approx W * 6000\lambda^2$



# Relative Areas

- ▶ Logic Area =  $(2^k * N) * 1000\lambda^2$
- ▶ Interconnect Area
  - ▶ Intra-Cluster Area =  $N^2 * \frac{k^2}{2} * 1000\lambda^2$
  - ▶ Cbox Area =  $W * \frac{k}{2} * N * 100\lambda^2$
  - ▶ Sbox Area =  $W * 6000\lambda^2$

## Relative Areas (Assume $k = 4$ )

- ▶ Logic Area =  $(16 * N) * 1000\lambda^2$
- ▶ Interconnect Area
  - ▶ Intra-Cluster Area =  $8 * N^2 * 1000\lambda^2$
  - ▶ Cbox Area =  $4 * W * N * 100\lambda^2$
  - ▶ Sbox Area =  $W * 6000\lambda^2$

## Relative Areas (Assume $N = 8$ )

- ▶ Logic Area =  $128 * 1000\lambda^2$
- ▶ Interconnect Area
  - ▶ Intra-Cluster Area =  $512 * 1000\lambda^2$
  - ▶ Cbox Area =  $32 * W * 100\lambda^2$
  - ▶ Sbox Area =  $W * 6000\lambda^2$

## Relative Areas (Assume $W = 60$ )

- ▶ Logic Area =  $128 * 1000\lambda^2$
- ▶ Interconnect Area
  - ▶ Intra-Cluster Area =  $512 * 1000\lambda^2$
  - ▶ Cbox Area =  $192 * 1000\lambda^2$
  - ▶ Sbox Area =  $360 * 1000\lambda^2$

## Relative Areas (Relative Ratios)

- ▶ Logic Area =  $128 * 1000\lambda^2$  – 11%
- ▶ Interconnect Area
  - ▶ Intra-Cluster Area =  $512 * 1000\lambda^2$  – 46%
  - ▶ Cbox Area =  $192 * 1000\lambda^2$  – 17%
  - ▶ Sbox Area =  $360 * 1000\lambda^2$  – 23%

## Class Wrapup

- ▶ Interconnect is  $\approx 90\%$  of the FPGA area
- ▶ Building *models* of hardware is helpful in deriving insight on operation
- ▶ Often OK to waste some LUTs, to use wires more efficiently
- ▶ Analytical model shows that for most realistic chips, switch area dominates wiring area for reasonable values of  $W$