

Scheduling Examples

Nachiket Kapre

nachiket@uwaterloo.ca



Outline

- ▶ Scheduling under Area-Time Tradeoff Scenarios
- ▶ Scheduling with Xilinx DSP blocks (simplified)


Area-Time Tradeoffs

- ▶ Developers must Hold resources accountable for their inclusion
 - ▶ Resources cost area on a chip = \$\$\$
 - ▶ Is it worth the silicon cost to include a particular hardware resource?
- ▶ Two extremes:
 - ▶ Fully sequential (one resource of each type) is bare minimum, slow and cheap
 - ▶ Fully spatial (parallel) is the best performing, most expensive
- ▶ Intermediate cases possible, use extra resources wisely! → analysis and optimizations required

Polynomial $f = a \cdot x^3 + b \cdot y^2 + c \cdot z + d$


- ▶ Each input is an 8-bit unsigned number. Addition does overflow (extra output bit necessary)
- ▶ Expression has 3 additions and 6 multiplications!
 - ▶ Constraint: We are using 2-input add and 2-input multiply primitives
- ▶ Fully sequential design requires one multiplier + one adder
 - ▶ Latency = 9 cycles
 - ▶ Throughput = $\frac{1}{9}$
- ▶ Fully parallel design requires 3 adders and 6 multipliers
 - ▶ Latency = 4 cycles
 - ▶ Throughput = 1

Fully Spatial (Parallel) Design

 


- ▶ Throughput=1, Latency=4
- ▶ Clock Period= $\max(T_{*8}, T_{*16}, T_{*24}, T_{+17}, T_{+25}, T_{+33})$

Fully Sequential Design

 


- ▶ 1st Cycle $\rightarrow t1 \leq a \times x$
- ▶ 2nd Cycle $\rightarrow t1 \leq t1 \times x$
- ▶ 3rd Cycle $\rightarrow t1 \leq t1 \times x$
- ▶ 4th Cycle $\rightarrow t2 \leq b \times y$
- ▶ 5th Cycle $\rightarrow t2 \leq t2 \times y$
- ▶ 6th Cycle $\rightarrow t3 \leq c \times z$
- ▶ 7th Cycle $\rightarrow t3 \leq t3 + d$
- ▶ 8th Cycle $\rightarrow t3 \leq t3 + t2$
- ▶ 9th Cycle $\rightarrow f \leq t3 + t1$

Fully Sequential Design

 


- ▶ 1st Cycle $\rightarrow t1 \leq a \times x$
- ▶ 2nd Cycle $\rightarrow t1 \leq t1 \times x$
- ▶ 3rd Cycle $\rightarrow t1 \leq t1 \times x$
- ▶ 4th Cycle $\rightarrow t2 \leq b \times y$
- ▶ 5th Cycle $\rightarrow t2 \leq t2 \times y$
- ▶ 6th Cycle $\rightarrow t3 \leq c \times z$
- ▶ 7th Cycle $\rightarrow t3 \leq t3 + d$
- ▶ 8th Cycle $\rightarrow t3 \leq t3 + t2$
- ▶ 9th Cycle $\rightarrow f \leq t3 + t1$

Fully Sequential Design

 


- ▶ 1st Cycle $\rightarrow t1 \leq a \times x$
- ▶ 2nd Cycle $\rightarrow t1 \leq t1 \times x$
- ▶ 3rd Cycle $\rightarrow t1 \leq t1 \times x$
- ▶ 4th Cycle $\rightarrow t2 \leq b \times y$
- ▶ 5th Cycle $\rightarrow t2 \leq t2 \times y$
- ▶ 6th Cycle $\rightarrow t3 \leq c \times z$
- ▶ 7th Cycle $\rightarrow t3 \leq t3 + d$
- ▶ 8th Cycle $\rightarrow t3 \leq t3 + t2$
- ▶ 9th Cycle $\rightarrow f \leq t3 + t1$

Fully Sequential Design

 


- ▶ 1st Cycle $\rightarrow t1 \leq a \times x$
- ▶ 2nd Cycle $\rightarrow t1 \leq t1 \times x$
- ▶ 3rd Cycle $\rightarrow t1 \leq t1 \times x$
- ▶ 4th Cycle $\rightarrow t2 \leq b \times y$
- ▶ 5th Cycle $\rightarrow t2 \leq t2 \times y$
- ▶ 6th Cycle $\rightarrow t3 \leq c \times z$
- ▶ 7th Cycle $\rightarrow t3 \leq t3 + d$
- ▶ 8th Cycle $\rightarrow t3 \leq t3 + t2$
- ▶ 9th Cycle $\rightarrow f \leq t3 + t1$

Fully Sequential Design

 


- ▶ 1st Cycle $\rightarrow t1 \leq a \times x$
- ▶ 2nd Cycle $\rightarrow t1 \leq t1 \times x$
- ▶ 3rd Cycle $\rightarrow t1 \leq t1 \times x$
- ▶ 4th Cycle $\rightarrow t2 \leq b \times y$
- ▶ 5th Cycle $\rightarrow t2 \leq t2 \times y$
- ▶ 6th Cycle $\rightarrow t3 \leq c \times z$
- ▶ 7th Cycle $\rightarrow t3 \leq t3 + d$
- ▶ 8th Cycle $\rightarrow t3 \leq t3 + t2$
- ▶ 9th Cycle $\rightarrow f \leq t3 + t1$

Fully Sequential Design

 


- ▶ 1st Cycle $\rightarrow t1 \leq a \times x$
- ▶ 2nd Cycle $\rightarrow t1 \leq t1 \times x$
- ▶ 3rd Cycle $\rightarrow t1 \leq t1 \times x$
- ▶ 4th Cycle $\rightarrow t2 \leq b \times y$
- ▶ 5th Cycle $\rightarrow t2 \leq t2 \times y$
- ▶ 6th Cycle $\rightarrow t3 \leq c \times z$
- ▶ 7th Cycle $\rightarrow t3 \leq t3 + d$
- ▶ 8th Cycle $\rightarrow t3 \leq t3 + t2$
- ▶ 9th Cycle $\rightarrow f \leq t3 + t1$

Fully Sequential Design

 


- ▶ 1st Cycle $\rightarrow t1 \leq a \times x$
- ▶ 2nd Cycle $\rightarrow t1 \leq t1 \times x$
- ▶ 3rd Cycle $\rightarrow t1 \leq t1 \times x$
- ▶ 4th Cycle $\rightarrow t2 \leq b \times y$
- ▶ 5th Cycle $\rightarrow t2 \leq t2 \times y$
- ▶ 6th Cycle $\rightarrow t3 \leq c \times z$
- ▶ 7th Cycle $\rightarrow t3 \leq t3 + d$
- ▶ 8th Cycle $\rightarrow t3 \leq t3 + t2$
- ▶ 9th Cycle $\rightarrow f \leq t3 + t1$

Fully Sequential Design

 


- ▶ 1st Cycle $\rightarrow t1 \leq a \times x$
- ▶ 2nd Cycle $\rightarrow t1 \leq t1 \times x$
- ▶ 3rd Cycle $\rightarrow t1 \leq t1 \times x$
- ▶ 4th Cycle $\rightarrow t2 \leq b \times y$
- ▶ 5th Cycle $\rightarrow t2 \leq t2 \times y$
- ▶ 6th Cycle $\rightarrow t3 \leq c \times z$
- ▶ 7th Cycle $\rightarrow t3 \leq t3 + d$
- ▶ 8th Cycle $\rightarrow t3 \leq t3 + t2$
- ▶ 9th Cycle $\rightarrow f \leq t3 + t1$

Fully Sequential Design

 

- ▶ 1st Cycle $\rightarrow t1 \leq a \times x$
- ▶ 2nd Cycle $\rightarrow t1 \leq t1 \times x$
- ▶ 3rd Cycle $\rightarrow t1 \leq t1 \times x$
- ▶ 4th Cycle $\rightarrow t2 \leq b \times y$
- ▶ 5th Cycle $\rightarrow t2 \leq t2 \times y$
- ▶ 6th Cycle $\rightarrow t3 \leq c \times z$
- ▶ 7th Cycle $\rightarrow t3 \leq t3 + d$
- ▶ 8th Cycle $\rightarrow t3 \leq t3 + t2$
- ▶ 9th Cycle $\rightarrow f \leq t3 + t1$

Fully Sequential Design

 


- ▶ 1st Cycle $\rightarrow t1 \leq a \times x$
- ▶ 2nd Cycle $\rightarrow t1 \leq t1 \times x$
- ▶ 3rd Cycle $\rightarrow t1 \leq t1 \times x$
- ▶ 4th Cycle $\rightarrow t2 \leq b \times y$
- ▶ 5th Cycle $\rightarrow t2 \leq t2 \times y$
- ▶ 6th Cycle $\rightarrow t3 \leq c \times z$
- ▶ 7th Cycle $\rightarrow t3 \leq t3 + d$
- ▶ 8th Cycle $\rightarrow t3 \leq t3 + t2$
- ▶ 9th Cycle $\rightarrow f \leq t3 + t1$

Intermediate Design Points

- ▶ Often, we can afford to allocate more resources → where to spend this resource?
- ▶ Consider design alternatives → add more multipliers, and/or adders, and/or registers
- ▶ Among alternatives, pick the one that most improves throughput (or latency, if that is the designer constraint)

Generic design template

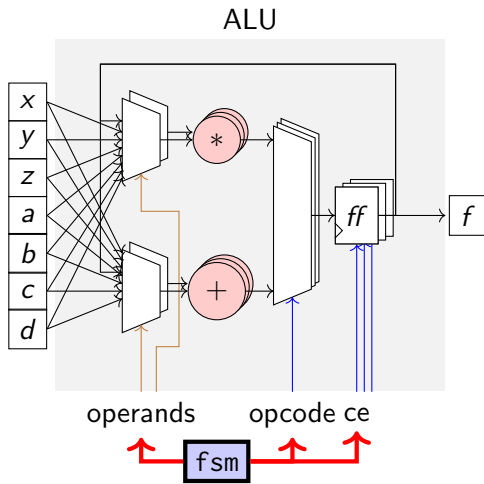

Schedule Table for one multiplier, one adder

Cycle	Operators	
	add_0	$mult_0$
0	-	$a \cdot x$
1	-	$a \cdot x^2$
2	-	$a \cdot x^3$
3	$a \cdot x^3 + d$	$b \cdot y$
4	-	$b \cdot y^2$
5	$a \cdot x^3 + b \cdot y^2 + d$	$c \cdot z$
6	$a \cdot x^3 + b \cdot y^2 + c \cdot z + d$	-

- ▶ Latency = 7 cycles, Throughput = $\frac{1}{7}$
- ▶ Problem: Lot of wasted cycles on the adder!
- ▶ Efficiency = Useful Cycles/Total Cycles = $\frac{9}{14}$

Schedule Table for two multipliers, one adder

Cycle	Operators		
	add_0	$mult_0$	$mult_1$
0	-	$a \cdot x$	$b \cdot y$
1	-	$a \cdot x^2$	$b \cdot y^2$
2	$b \cdot y^2 + d$	$a \cdot x^3$	$c \cdot z$
3	$a \cdot x^3 + b \cdot y^2 + d$	-	-
4	$a \cdot x^3 + b \cdot y^2 + c \cdot z + d$	-	-

- ▶ Latency = 5 cycles, Throughput = $\frac{1}{5}$
- ▶ Efficiency = $\frac{9}{15}$


Schedule Table for three multipliers, one adder

Cycle	Operators			
	add_0	$mult_0$	$mult_1$	$mult_2$
0	-	$a \cdot x$	$b \cdot y$	$c \cdot z$
1	$c \cdot z + d$	$a \cdot x^2$	$b \cdot y^2$	-
2	$b \cdot y^2 + c \cdot z + d$	$a \cdot x^3$	-	-
3	$a \cdot x^3 + b \cdot y^2 + c \cdot z + d$	-	-	-

- ▶ Latency = 4 cycles, Throughput = $\frac{1}{4}$
- ▶ Efficiency = $\frac{9}{16}$

Area-Time Tradeoff Visualization

 - ▶ **Assumption:** Area of multiplier = 3*Area of adder
 - ▶ A = one multiplier + one adder = 4 units
 - ▶ B = two multipliers + one adder = 7 units
 - ▶ C = three multipliers + one adder = 10 units
 - ▶ D = six multipliers + three adders = 21 units



Scheduling with Variable Resource Constraints

- ▶ Area-Time tradeoffs are at the heart of hardware design → every piece of hardware must justify its existence → millions of dollars of manufacturing!
- ▶ Aggressively schedule to minimize latency, boost throughput
- ▶ Always check if replicating cheap block is a possibility?


Replication Scenarios – Good

- ▶ Replicate A to fit the area occupied by C
 - ▶ $\text{Area}(C) = 10$ units, $\text{Area}(A) = 4$ units.
 - ▶ $\text{Area}(\text{two copies of } A) = 4 \text{ units} \times 2 = 8 \text{ units}$
 - ▶ Thus, we can easily fit $2 \times A$ in area of one C
- ▶ Check throughputs:
 - ▶ Throughput of A = $\frac{1}{7}$
 - ▶ Throughput of C = $\frac{1}{5}$
 - ▶ Throughput of two copies of A = $2 \times \frac{1}{7} = \frac{1}{3.5}$
 - ▶ Thus, $\text{Throughput}(\text{two copies of } A) > \text{Throughput}(C)$
 - ▶ $\frac{1}{3.5} > \frac{1}{5}$
- ▶ **What this means?** If you can afford to pay for C, just implement instances of A instead!

Replication Scenarios – Bad


- ▶ Replicate A to fit the area occupied by D
 - ▶ $\text{Area}(D) = 21$ units, $\text{Area}(A) = 4$ units
 - ▶ $\text{Area}(\text{five copies of } A) = 4 \text{ units} \times 5 = 20 \text{ units}$
 - ▶ Thus, we can easily fit $5 \times A$ in area of one C
- ▶ Check throughputs:
 - ▶ Throughput of A = $\frac{1}{7}$
 - ▶ Throughput of D = 1
 - ▶ Throughput of five copies of A = $5 \times \frac{1}{7} = \frac{5}{7}$
 - ▶ Thus, $\text{Throughput}(\text{five copies of } A) < \text{Throughput}(D)$
 - ▶ $\frac{5}{7} < 1$
- ▶ **What this means?** If you can afford to pay for D, just implement D instead of being a cheapskate and replicating A!

Scheduling with Fixed-Function Units

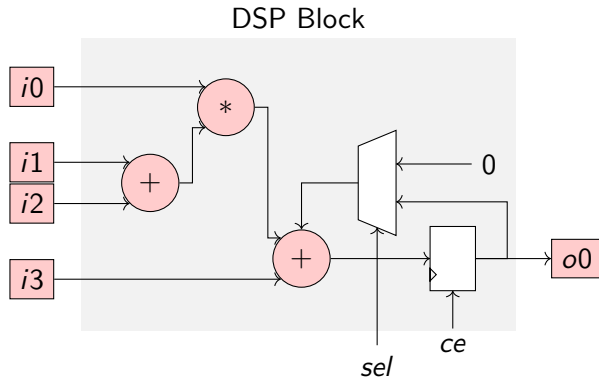

- ▶ Modern FPGAs contain add-multiply blocks that can be programmed to suite customer requirements
- ▶ Embedded FPGA blocks are fast structures → more on FPGA architecture after midterm

Scheduling with Fixed-Function Units

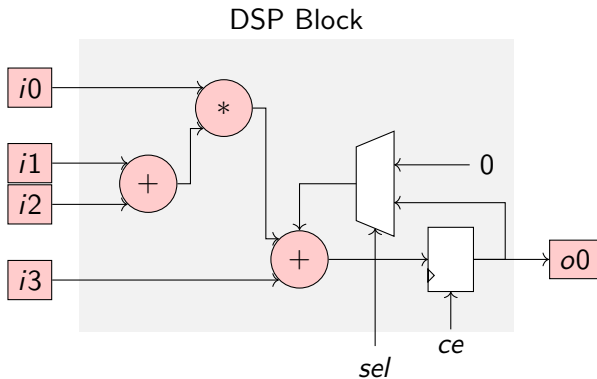


- ▶ Three arithmetic units →
 - ▶ pre-adder ($i1 + i2$)
 - ▶ multiplier ($i0 \times (i1 + i2)$)
 - ▶ accumulator ($o0 = o0 + i0 \times (i1 + i2) + i3$)
- ▶ Programmable ce and sel inputs to steer and control data inside the DSP

Computational Folding over FPGA DSPs


- ▶ Time multiplexing of a DSP block is an example of scheduling
- ▶ Another word for it → computational folding
 - ▶ Why? Because computational origami was taken
- ▶ Split your input expression into multiple DSP operations
- ▶ Precision of adders and multipliers determine how to slice up operations → for this lecture, assume sufficient

Types of Operations possible

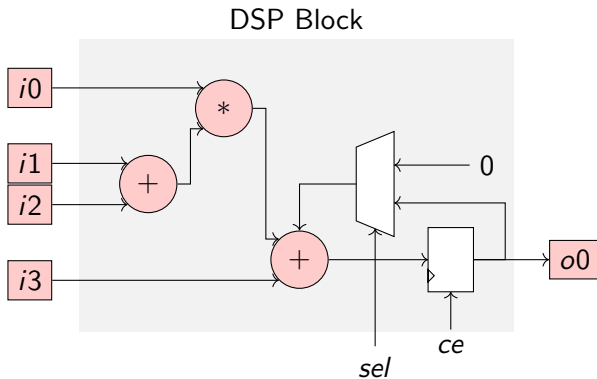


Highly flexible datapath


Types of Operations possible

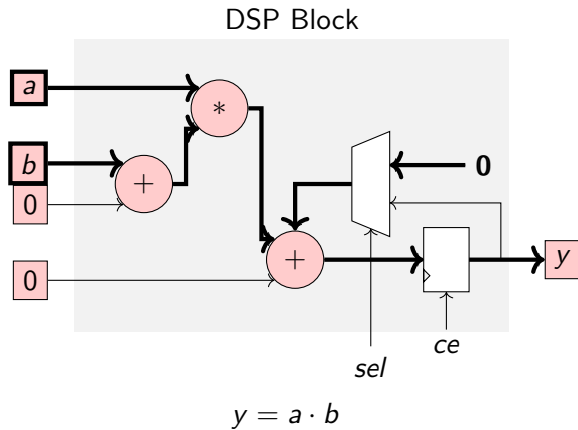


Types of Operations possible

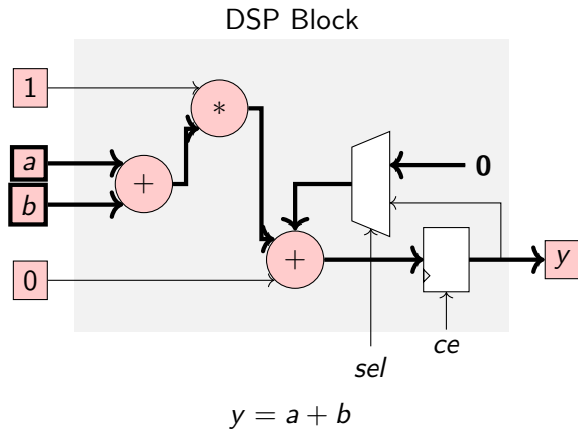

Types of Operations possible

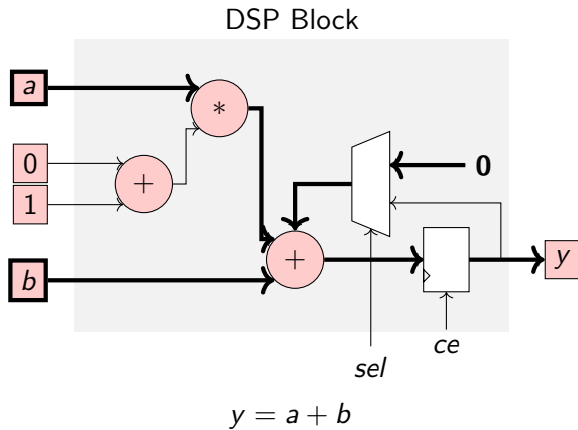


Types of Operations possible

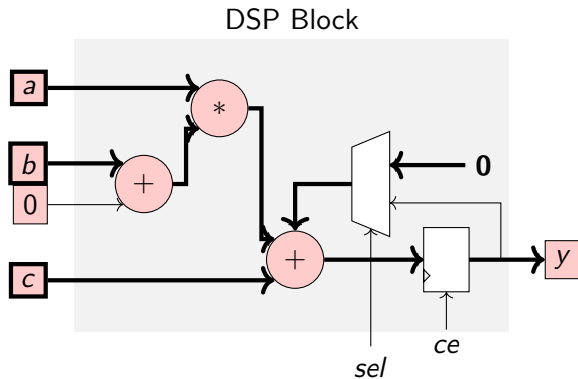


$$y = a \cdot b + c$$

 Mapping poly $a \cdot x^2 + b \cdot x + c$ to a DSP




Cycle	Intra-DSP Operations			Output $o0 = accum$
	$preadd(p)$	$mult(m)$	$accum$	
0	$a + 0$	$p \cdot x$	$m + 0 + 0$	$a \cdot x$
1	$a \cdot x + 0$	$p \cdot x$	$m + 0 + 0$	$a \cdot x^2$
2	$b + 0$	$p \cdot x$	$m + o0 + 0$	$a \cdot x^2 + b \cdot x$
3	$0 + 0$	$p \cdot x$	$m + o0 + c$	$a \cdot x^2 + b \cdot x + c$

 Mapping poly $a \cdot x^2 + b \cdot x + c$ to a DSP




Cycle	Intra-DSP Operations			Output $o0 = accum$
	$preadd(p)$	$mult(m)$	$accum$	
0	$a + 0$	$p \cdot x$	$m + 0 + 0$	$a \cdot x$
1	$a \cdot x + 0$	$p \cdot x$	$m + 0 + 0$	$a \cdot x^2$
2	$b + 0$	$p \cdot x$	$m + o0 + 0$	$a \cdot x^2 + b \cdot x$
3	$0 + 0$	$p \cdot x$	$m + o0 + c$	$a \cdot x^2 + b \cdot x + c$

 Mapping poly $a \cdot x^2 + b \cdot x + c$ to a DSP




Cycle	Intra-DSP Operations			Output $o0 = accum$
	$preadd(p)$	$mult(m)$	$accum$	
0	$a + 0$	$p \cdot x$	$m + 0 + 0$	$a \cdot x$
1	$a \cdot x + 0$	$p \cdot x$	$m + 0 + 0$	$a \cdot x^2$
2	$b + 0$	$p \cdot x$	$m + o0 + 0$	$a \cdot x^2 + b \cdot x$
3	$0 + 0$	$p \cdot x$	$m + o0 + c$	$a \cdot x^2 + b \cdot x + c$

 Mapping poly $a \cdot x^2 + b \cdot x + c$ to a DSP




Cycle	Intra-DSP Operations			Output $o0 = accum$
	$preadd(p)$	$mult(m)$	$accum$	
0	$a + 0$	$p \cdot x$	$m + 0 + 0$	$a \cdot x$
1	$a \cdot x + 0$	$p \cdot x$	$m + 0 + 0$	$a \cdot x^2$
2	$b + 0$	$p \cdot x$	$m + o0 + 0$	$a \cdot x^2 + b \cdot x$
3	$0 + 0$	$p \cdot x$	$m + o0 + c$	$a \cdot x^2 + b \cdot x + c$

 Mapping poly $a \cdot x^2 + b \cdot x + c$ to a DSP




Cycle	Intra-DSP Operations			Output $o0 = accum$
	$preadd(p)$	$mult(m)$	$accum$	
0	$a + 0$	$p \cdot x$	$m + 0 + 0$	$a \cdot x$
1	$a \cdot x + 0$	$p \cdot x$	$m + 0 + 0$	$a \cdot x^2$
2	$b + 0$	$p \cdot x$	$m + o0 + 0$	$a \cdot x^2 + b \cdot x$
3	$0 + 0$	$p \cdot x$	$m + o0 + c$	$a \cdot x^2 + b \cdot x + c$

 Mapping poly $a \cdot x^2 + b \cdot x + c$ to a DSP





Cycle	IO Table			
	$i0$	$i1$	$i2$	$i3$
0	x	a	0	0
1	x	$a \cdot x$	0	0
2	x	b	0	0
3	0	-	0	c

 Mapping poly $a \cdot x^2 + b \cdot x + c$ to a DSP




Cycle	Selection	
	<i>sel</i>	<i>ce</i>
0	0	1
1	0	1
2	1	1
3	1	1

  Mapping poly $a \cdot x^2 + b \cdot x + c$ to a DSP




- ▶ $y_0 = a \cdot x$
- ▶ $y_1 = a \cdot x^2$
- ▶ $y_2 = a \cdot x^2 + b \cdot x$
- ▶ $y = a \cdot x^2 + b \cdot x + c$

 Mapping poly $a \cdot x^2 + b \cdot x + c$ to a DSP (Optimized)




Cycle	Intra-DSP Operations			Output $o0 = accum$
	$preadd(p)$	$mult(m)$	$accum$	
0	$a + 0$	$p \cdot x$	$m + 0 + b$	$a \cdot x + b$
1	$(a \cdot x + b) + 0$	$p \cdot x$	$m + 0 + c$	$(a \cdot x + b) \cdot x + c$

 Mapping poly $a \cdot x^2 + b \cdot x + c$ to a DSP (Optimized)




Cycle	Intra-DSP Operations			Output $o0 = accum$
	$preadd(p)$	$mult(m)$	$accum$	
0	$a + 0$	$p \cdot x$	$m + 0 + b$	$a \cdot x + b$
1	$(a \cdot x + b) + 0$	$p \cdot x$	$m + 0 + c$	$(a \cdot x + b) \cdot x + c$

 Mapping poly $a \cdot x^2 + b \cdot x + c$ to a DSP (Optimized)




Cycle	Intra-DSP Operations			Output $o0 = accum$
	$preadd(p)$	$mult(m)$	$accum$	
0	$a + 0$	$p \cdot x$	$m + 0 + b$	$a \cdot x + b$
1	$(a \cdot x + b) + 0$	$p \cdot x$	$m + 0 + c$	$(a \cdot x + b) \cdot x + c$

 Mapping poly $a \cdot x^2 + b \cdot x + c$ to a DSP (Optimized)





Cycle	IO Table			
	$i0$	$i1$	$i2$	$i3$
0	x	a	0	b
1	x	$a \cdot x + b$	0	c

 Mapping poly $a \cdot x^2 + b \cdot x + c$ to a DSP (Optimized)



Cycle	Selection	
	sel	ce
0	0	1
1	0	1

  Mapping poly $a \cdot x^2 + b \cdot x + c$ to a DSP (Optimized)



► $y0 = a \cdot x + b$

► $y = (a \cdot x + b) \cdot x + c$

Mapping Technique

- ▶ Different ways to perform algebraic factorization
- ▶ Core DSP computes $o0 = (i1 + i2) \cdot i0 + i3 + o0$
- ▶ Attempt to extract this expression from your application
- ▶ Use as many multiplier and adder blocks in same cycle
- ▶ External feedback sometimes necessary!
- ▶ Minimize the number of cycles

Class Wrapup

- ▶ Area-Time tradeoffs fundamental aspect of hardware design
- ▶ Resources must be introduced carefully with high utilization
- ▶ Reduce the number of cycles, and enhance utilization of hardware resources
- ▶ FPGAs today ship with DSP blocks that contain fast multiply and addition blocks
→ scheduling is needed to use them properly.